

NAME: KAPAROTU VENKATA SURYA THARANI
USN: 22BTRAD018

EXP9- LOGIC GATES

AIM: To verify the truth tables of NOT, AND and OR gates using Diodes and Transistor.

COMPONENTS: Diodes, Transistor, Resistors and LED, DC Power supply, multi-meter.


Simulation tool: <https://www.tinkercad.com/>

Use this link to simulate the circuit diagrams which are shown below for NOT, AND, and OR gates.

PROCEDURE:

1. Use components and make the circuit connections as per the circuit diagram shown below.
2. Turn on power to your experimental circuit.
3. Apply all four possible combinations of input voltages at A and B, Record the output voltage and status of LED.
4. For each input combination, note the logic state of the output, as indicated by the LED (ON = 1; OFF = 0), and record that result in the table.
5. Compare your results with the truth table of a logic "NOT"/ "AND"/ "OR"/ operation.
6. Submit the worksheets in to LMS along with the image of simulation.

CIRCUIT DIAGRAM:

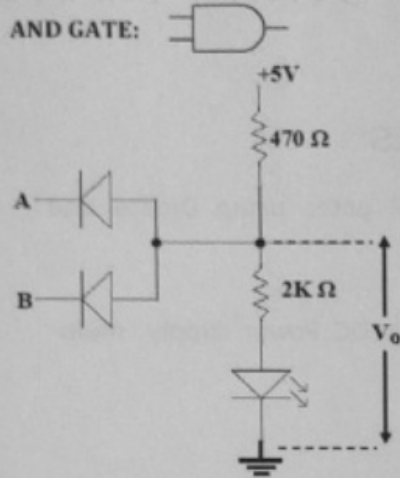


Truth table		
A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Logic status (LED)		
A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Logic status (Volts)		
A	B	$Y = A \cdot B$
0	0	0.6
0	1	0.6
1	0	0.6
1	1	5.0

NOT GATE:

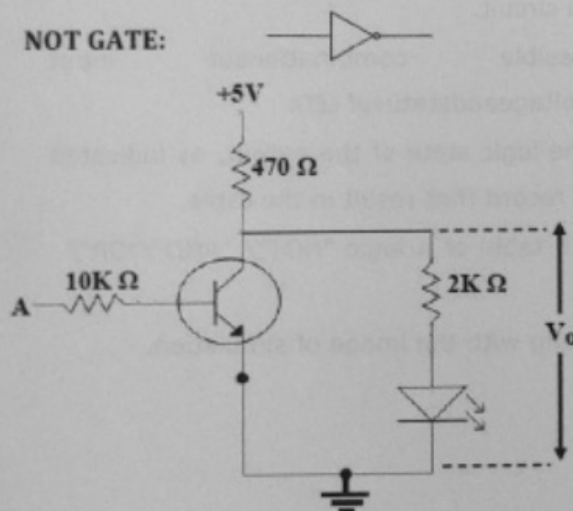


Truth table	
A	$Y = \bar{A}$
0	1
1	0

Logic status (LED)	
A	$Y = \bar{A}$
0	1
1	0

Logic status (Volts)	
A	$Y = \bar{A}$
0	5.0
1	0.1

OR GATE:

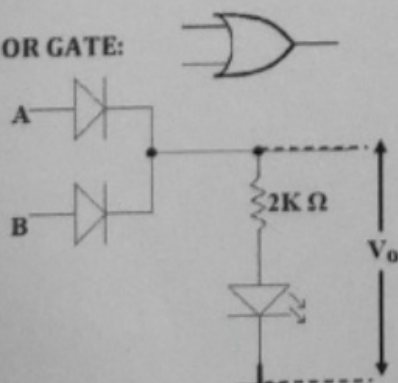

Truth table		
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Logic status (LED)		
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Logic status (Volts)		
A	B	$Y = A + B$
0	0	0
0	1	4.3
1	0	4.3
1	1	4.3

Result:

The truth tables of NOT, AND, and OR gates are verified. Respective input and output voltages are measured and are tabulated.

Note: Submit the worksheet in to LMS along with the simulation image.